


THE

# BALLAST TUBE



HANDBOOK
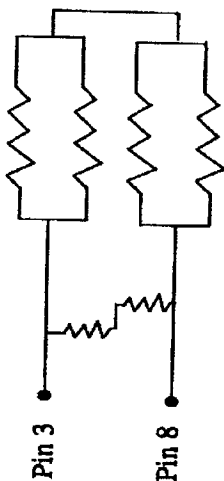
## Resistor Substitution for Ballast

The L-40-S can be eliminated by the following set of six five watt resistors:



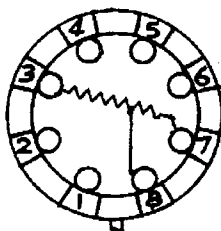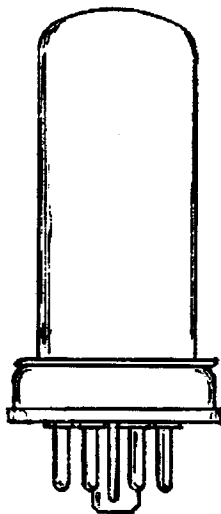Use a transformer for the six volt pilot lights; and if you have ballast resistor problems be sure to get a copy of Anthony Jacobi's new book, *The Ballast Tube Handbook*, listing over 4000 tubes. \$10.95, No. B-573, from Antique Electronic Supply in Tempe and other suppliers.



Compiled by A. P. Jacobi